

Introduction to Sequential Digital Systems

By
Kolawole Yusuf Obiwusi

Sequential Logic Circuits

- Output depends on current inputs
- Output also depends on past inputs (memory)
- Can remember previous states
- Uses feedback paths

Memory Elements

- Sequential circuits contain memory elements such as:
 - Flip-flops
 - Latches
 - Registers
- These elements store binary data (0 or 1).

Structure of a Sequential Circuit

- Inputs → Combinational Logic → Memory → Output
- • Logic processes inputs
- • Memory stores state
- • Feedback influences future output

Flip-Flop

- Basic memory device
- Stores one bit of information
- Triggered by a clock signal
- Building block of registers and counters

D Flip-Flop

- D input represents data
- On clock edge, $Q = D$
- Stores one bit
- \bar{Q} is inverted output

Combinational vs Sequential Circuits

- Combinational:
 - No memory
 - Output depends only on inputs
- Sequential:
 - Has memory
 - Output depends on present and past inputs

4-Bit Register

- Consists of four flip-flops
- Stores four bits of data
- All flip-flops share same clock
- Used in CPU data storage

Clock Signal

- Periodic timing pulse
- Synchronizes circuit operation
- Rising or falling edge triggered
- Controls system speed

Timing Diagram (D Flip-Flop)

- Shows relationship between CLK, D, and Q
- Q changes only at clock edge
- Used for timing analysis

4-Bit Binary Counter

- Counts from 0 to 15
- Changes state on each clock pulse
- Used in timers and digital clocks

Finite State Machine (FSM)

- System with finite number of states
- Transitions depend on inputs
- Controlled by clock
- Used in control systems

Importance in Computer Systems

- CPU operation
- Data storage
- Timing and control
- Instruction sequencing

Summary

- Sequential Logic = Logic + Memory + Clock
 - Logic processes data
 - Memory stores state
 - Clock synchronizes operations

Thank You